

Electricity: switches, conductors and a quiz buzzer

energy-forces

What you need: 1.5V battery with holder · buzzer or bulb with holder · wires with crocodile clips · aluminium foil pieces and paperclips · card rectangles for the quiz or track base · scissors

Words to use

Switch · Closed loop · Contact points

Draw what I see

What I notice

What I found out

