

Electricity: switches, conductors and a quiz buzzer

energy-forces

Words to use

Switch · Closed loop · Conductor · Contact points

Draw the circuit your group built. Label the battery, the buzzer or bulb, the wires, and the two places that touch to switch it on.

What job does this circuit do? Write one sentence.

